NASA TECH BRIEF



NASA Tech Briefs announce new technology derived from the U.S. space program. They are issued to encourage commercial application. Tech Briefs are available on a subscription basis from the Clearinghouse for Federal Scientific and Technical Information, Springfield, Virginia 22151. Requests for individual copies or questions relating to the Tech Brief program may be directed to the Technology Utilization Division, NASA, Code UT, Washington, D.C. 20546.

Improved Low Cost AC-to-DC Converter

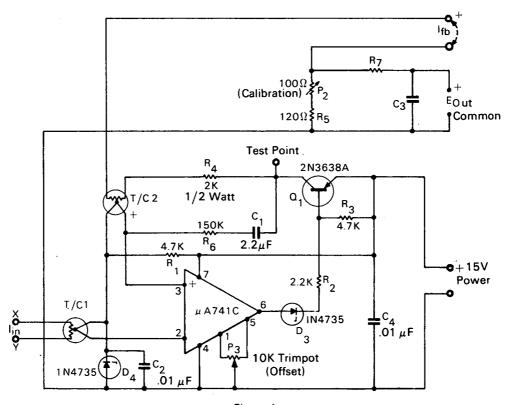


Figure 1


A low-cost circuit has been designed to convert an rms, ac voltage to a proportional dc voltage with good accuracy (± 1 to ± 1.5 percent) over a voltage range of approximately 6:1. The converter, which incorporates a pair of vacuum thermocouples (V-T/C's) in a dc feedback circuit, exhibits a temperature coefficient of approximately +0.01 to -0.04 percent over the temperature range from 20° to 165° F. This converter can be built at about one-quarter the cost of a similar commercially available circuit which

operates at a ± 1 percent accuracy over a 10:1 range and should be of interest to manufacturers and users of instruments, such as X-Y plotters and data recorders, that operate on dc voltages.

Figure 1 shows a circuit schematic with illustrative component values. The input T/C 1 is a 1 mA type used for current-to-voltage conversion in the input loop; T/C 2 is a 5 mA type used in the feedback loop. Each of these T/C's is contained in a glass bead and is electrically insulated from the heater to 100 volts

(continued overleaf)

peak. The T/C's are closely matched to avoid non-linearity between input and output. A damping and filtering network in the negative feedback loop consists of a 150 kilohm resistor (R_6) in series with a 2.2 μ F, 25V capacitor (C_1). Transistor Q_1 provides additional loop gain and also provides a voltage shift to allow the use of a grounded power supply. Resistor R_4 protects T/C 2 from burnout. A 10 kilohm potentiometer (P_3) serves as a dc offset adjustment. A 0 to 5 mA dc meter may be placed in series with T/C 2 as a permanent monitor. If a meter is not used, the terminals must be shorted. The output terminals of the circuit are connected in series with resistor R_5 and calibration potentiometer P_2 . The latter is adjusted to provide a 1 V dc output when a

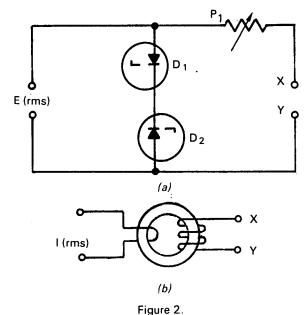

normal maximum of 3 V rms is applied at the input, and P₁ (Figure 2a) is adjusted for a current of 1.2 mA through T/C 1. Zener diodes D1 and D2 (Figure 2a) protect the T/C 1 heater against burnout. Although T/C 1 has a nominal current rating of 1 mA, the slight overcurrent (1.2 mA) will ensure a higher T/C output voltage and greater overall accuracy.

Figure 2b shows an rms current-input circuit that can be used in place of the rms voltage input to the converter circuit. A current transformer with a ratio $X_A / T_{/Cl}$ (where X_A = the maximum current to be measured) is substituted for the input circuit of Figure 2a.

To remove noise from the output signal (E_{out}) , a filter network may be added $(R_7 \ C_3 \ in \ Figure \ 1)$. Such a network should maintain or reflect a low impedance $(\le 2 \ kilohms)$ to the output terminals. The dc voltage output of this converter circuit is proportional to the rms current input. Because the thermocouples are insulated from the heaters to 100 V peak, there are no common-mode problems, and the output can be connected directly to the desired equipment (e.g., data system or recorder).

Note:

Requests for further information may be directed to:

Technology Utilization Officer NASA Pasadena Office 4800 Oak Grove Drive Pasadena. California Reference: TSP70-10076

Patent status:

No patent action is contemplated by NASA.

Source: H. C. Cremer of Caltech/JPL under contract to NASA Pasadena Office (NPO-11055)